

Digital Systems I

Computer Assignment #2


Basic Switch and Gate Structures in SystemVerilog

Amirali Dehghani

SID: 810102443


Introduction

This is an image of the project that I have created in ModelSim for the simulation of my circuit.

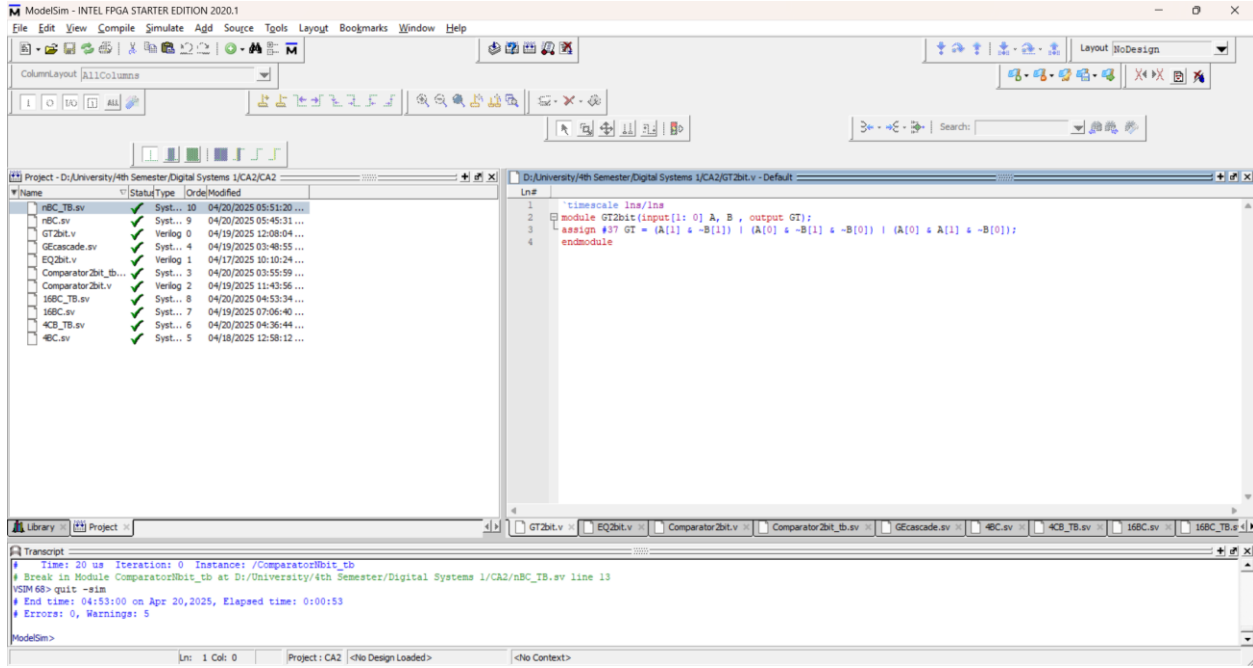

Question 1

Calculating gates delay on paper

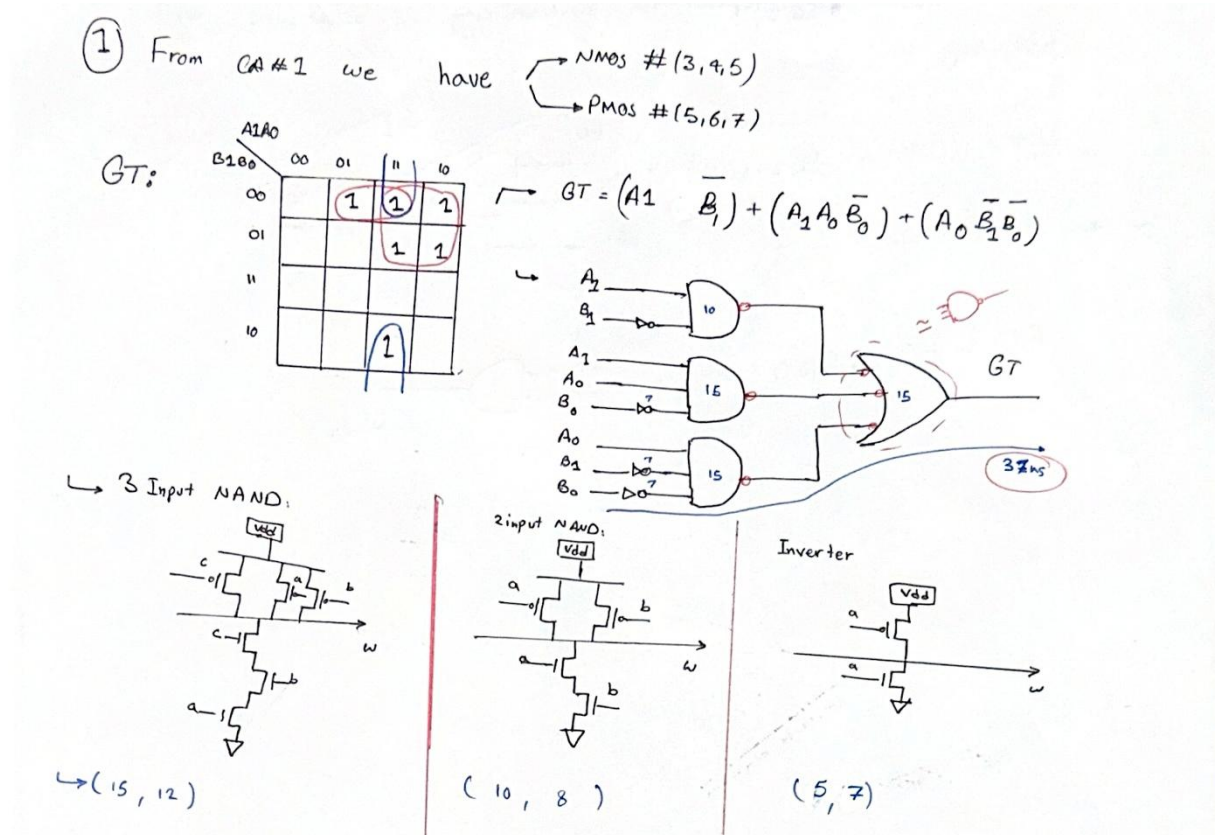

Code

```




1 `timescale 1ns/1ns
2 module GT2bit(input [1: 0] A, B , output GT);
3 assign #37 GT = (A[1] & ~B[1]) | (A[0] & ~B[1] & ~B[0]) | (A[0] & A[1] & ~B[0]);
4 endmodule

```

Question 2

Calculating gates delay on paper

② EQ:

   

Code

```

1  `timescale 1ns/1ns
2  module EQ2bit(input[1: 0] A, B , output EQ);
3  assign #49 EQ = (~A[1] | B[1]) & (A[1] | ~B[1]) & (~A[0] | B[0]) & (A[0] | ~B[0]);
4  endmodule

```

Question 3

For this part, because I have used GT2bit and EQ2bit modules, I expect 49ns delay as my 2-bit comparator's worst-case delay. Because it is between these 2 modules and EQ2bit has higher delay ($49 > 37$).

Code

```
1  `timescale 1ns/1ns
2  module Comparator2bit(input  [1:0] A, B, output GT, EQ);
3      GT2bit gt(.A(A), .B(B), .GT(GT));
4      EQ2bit eq(.A(A), .B(B), .EQ(EQ));
5  endmodule
```

Testbench

```
1  `timescale 1ns/1ns
2  module Comparator2bit_tb();
3      logic [1:0] A, B;
4      logic GT, EQ;
5      Comparator2bit uut(.A(A), .B(B), .GT(GT), .EQ(EQ));
6      initial begin
7          repeat (20) begin
8              A = $random() % 4;
9              B = $random() % 4;
10             #103;
11         end
12         $stop;
13     end
14 endmodule
```


Output



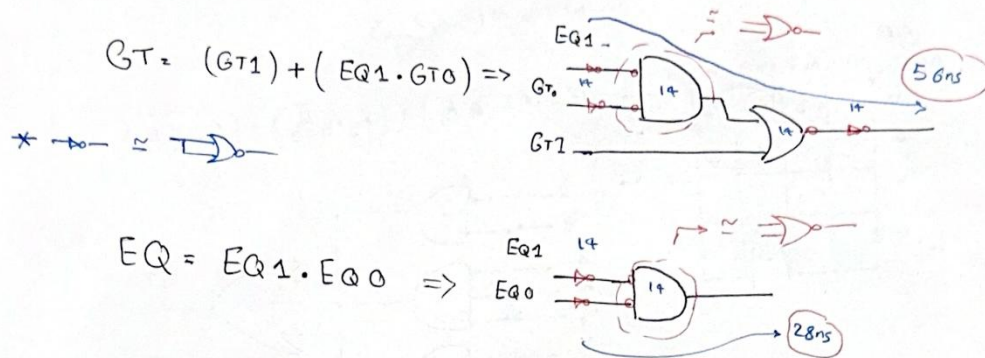Question 4

Building circuit on paper

④ From CA #1 we have 2-Input NOR with (10,14) delay and 3-input OAI with (10,14) delay.



Code

```

1  `timescale 1ns/1ns
2  module GEcascade(input GT1, GT0, EQ1, EQ0, output logic GT, EQ);
3      assign #56 GT = (EQ1 & GT0) | GT1;
4      assign #28 EQ = EQ1 & EQ0;
5  endmodule

```

Question 5

For this part, because I have used Comparator2bit and GEcascade modules, I expect 105ns delay as my 4-bit comparator's worst-case delay. Because GEcascade needs the output of 2-bit Comparators so it is $49 + 56 = 105$. GEcascade's delay is 56ns because of the expressions and circuits that I explained and drew in [Question 4](#).

Code

```
1  `timescale 1ns/1ns
2  module Comparator4bit (input  [3:0] A, B, output GT, EQ);
3      wire GT1, EQ1, GT0, EQ0;
4      Comparator2bit hi (.A(A[3:2]), .B(B[3:2]), .GT(GT1), .EQ(EQ1));
5      Comparator2bit lo (.A(A[1:0]), .B(B[1:0]), .GT(GT0), .EQ(EQ0));
6      GEcascade ge(.GT1(GT1), .EQ1(EQ1), .GT0(GT0), .EQ0(EQ0), .GT(GT), .EQ(EQ));
7  endmodule
```

Testbench

```
1  `timescale 1ns/1ns
2  module Comparator4bit_tb;
3      logic [3:0] A, B;
4      logic GT, EQ;
5      Comparator4bit uut(.A(A), .B(B), .GT(GT), .EQ(EQ));
6      initial begin
7          repeat (20) begin
8              A = $random() % 16;
9              B = $random() % 16;
10             #211;
11         end
12         $stop;
13     end
14 endmodule
```

Output



Question 6

As I explained my idea about last part, I expect $56 + 105 = 161\text{ns}$ delay for 8-bit comparator and $161 + 56 = 217\text{ns}$ delay for 16-bit comparator.


Code

```
1  `timescale 1ns/1ns
2  module Comparator8bit(input[7:0] A, B, output GT, EQ);
3      wire GT1, EQ1, GT0, EQ0;
4      Comparator4bit hi (.A(A[7:4]), .B(B[7:4]), .GT(GT1), .EQ(EQ1));
5      Comparator4bit lo (.A(A[3:0]), .B(B[3:0]), .GT(GT0), .EQ(EQ0));
6      GEcascade ge(.GT1(GT1), .EQ1(EQ1), .GT0(GT0), .EQ0(EQ0), .GT(GT), .EQ(EQ));
7  endmodule
8
9  module Comparator16bit(input[15:0] A, B, output GT, EQ);
10     wire GT1, EQ1, GT0, EQ0;
11     Comparator8bit hi (.A(A[15:8]), .B(B[15:8]), .GT(GT1), .EQ(EQ1));
12     Comparator8bit lo (.A(A[7:0]), .B(B[7:0]), .GT(GT0), .EQ(EQ0));
13     GEcascade ge(.GT1(GT1), .EQ1(EQ1), .GT0(GT0), .EQ0(EQ0), .GT(GT), .EQ(EQ));
14 endmodule
```

Testbench

```
1  `timescale 1ns/1ns
2  module Comparator16bit_tb;
3      logic [15:0] A, B;
4      logic GT, EQ;
5      Comparator16bit uut(.A(A), .B(B), .GT(GT), .EQ(EQ));
6      initial begin
7          repeat (10) begin
8              A = $random() % (2**16);
9              B = $random() % (2**16);
10             #439;
11         end
12         $stop;
13     end
14 endmodule
```

Output

 

Question 7

In general, the delay for each n -bit comparator was $56 \cdot n + 49$. For each testbench, I chose the nearest to twice that delay. But here is kind of different because now we have a for loop. So here we have a 2-bit comparator and a GEcascade that iterates for $n/2$ times. So now I expect $105(n/2)$ for each one as worst-case delay. For example we have about 840ns delay for 16-bit comparator.

Code

```
1  `timescale 1ns/1ns
2  module ComparatorNbit #(parameter N = 16) (input [N-1:0] A, B, output GT, EQ);
3      logic [N/2-1:0] gt, eq;
4      assign gt[0] = 0;
5      assign eq[0] = 1;
6      genvar i;
7      generate
8          for (i = 0; i < N/2; i++) begin
9              logic gti, eqi;
10             Comparator2bit c2 (.A(A[N - 2*i - 1 -: 2]), .B(B[N - 2*i - 1 -: 2]), .GT(gti), .EQ(eqi));
11             GEcascade ge (.GT1(gt[i]), .EQ1(eqi), .GT0(gti), .EQ0(eqi), .GT(gt[i+1]), .EQ(eq[i+1]));
12         end
13     endgenerate
14     assign GT = gt[N/2-1];
15     assign EQ = eq[N/2-1];
16 endmodule
```

Testbench

```
1  `timescale 1ns/1ns
2  module ComparatorNbit_tb();
3      parameter N = 16;
4      logic [N-1:0] A, B;
5      logic GT, EQ;
6      ComparatorNbit #(N) uut(.A(A), .B(B), .GT(GT), .EQ(EQ));
7      initial begin
8          repeat (10) begin
9              A = $random() % (2**N);
10             B = $random() % (2**N);
11             #2000;
12         end
13         $stop;
14     end
15 endmodule
```

Output

