 


# Digital Systems I – CA1

Amirali Dehghani – 810102443

## Part 1


After the delay  $t_{pd} = 0.0024 \mu s$



using rows # (3, 4, 5)  
ones # (5, 6, 7)


→ worst case delay

$H(10, 14)$   
row # 10 6

 

# (10, 14)

② OAI using NOR

 


# (26, 28)  
# (32, 38)

```

`timescale 1ns/1ns
module myNor_switch(input a, b, output w);
supply1 vdd;
supply0 gnd;
wire j;
pmos #(5, 6, 7) T1(j, vdd, a), T2(w, j, b);
nmos #(3, 4, 5) T3(w, gnd, a), T4(w, gnd, b);
endmodule
////////////////////////////////////
`timescale 1ns/1ns
module myOAI_switch(input a, b, c, output w);
supply1 vdd; supply0 gnd;
wire i, j;
pmos #(5, 6, 7) T1(i, vdd, a), T2(w, i, b), T3(w, vdd, c);
nmos #(3, 4, 5) T4(j, gnd, a), T5(j, gnd, b), T6(w, j, c);
endmodule
////////////////////////////////////
`timescale 1ns/1ns
module TB_1 ();
reg a1=0,b1=0,c1=0,a2=1,b2=1;
wire w1, w2;
myOAI_switch cut1(a1,b1,c1,w1);
myNor_switch cut2(a2,b2,w2);
initial begin
#47
a1=1; b1=0; c1=0; a2=0; b2=1;
#47
a1=1; b1=1; c1=0; b2=0; a2=0;
#47
a1=1; b1=1; c1=1; a2=1; b2=0;
#47
a1=0; b1=0; c1=1; b2=0; a2=0;
#47
a1=1; b1=0; c1=1;
#91
$stop;
end
endmodule

```

 


## Part 2

```


`timescale 1ns/1ns
module myOAI_norGate(input a, b, c, output w);
  wire i, j, k;
  myNor_switch n1(a, b, i), n2(c, c, j), n3(i,j,k), n4(k, k, w);
endmodule
////////////////////////////////////
`timescale 1ns/1ns
module TB_2();
  reg aa = 0, bb = 1, cc = 1;
  wire ww;
  myOAI_norGate cut(aa, bb, cc, ww);
initial begin
  #47 aa = 1; bb = 0; cc = 0;
  #47 aa = 1; bb = 1; cc = 0;
  #47 aa = 1; bb = 1; cc = 1;
  #47 aa = 0; bb = 0; cc = 1;
  #47 aa = 1; bb = 0; cc = 1;
  #103 $stop;
end
endmodule

```

 


### Part 3

```
`timescale 1ns/1ns
module myOAI_boolalg (input a,b,c, output w);
    assign #(10, 14) w = ~(a|b)&c;
endmodule
////////////////////////////////////
`timescale 1ns/1ns
module TB_3();
    reg aa = 0, bb = 1, cc = 1;
    wire ww;
    myOAI_boolalg cut(aa, bb, cc, ww);
    initial begin
        #47 aa = 1; bb = 0; cc = 0;
        #47 aa = 1; bb = 1; cc = 0;
        #47 aa = 1; bb = 1; cc = 1;
        #47 aa = 0; bb = 0; cc = 1;
        #47 aa = 1; bb = 0; cc = 1;
        #53 $stop;
    end
endmodule
```

 
 
#### Part 4

```
`timescale 1ns/1ns
module TB_4();
reg aa = 0, bb = 0, cc = 0;
wire w1, w2, w3;
myOAI_switch cut1(aa, bb, cc, w1);
myOAI_norGate cut2(aa, bb, cc, w2);
myOAI_boolalg cut3(aa, bb, cc, w3);
initial begin
    #47 aa = 1; bb = 0; cc = 0;
    #47 aa = 1; bb = 1; cc = 0;
    #47 aa = 1; bb = 1; cc = 1;
    #47 aa = 0; bb = 0; cc = 1;
    #47 aa = 1; bb = 0; cc = 1;
    repeat(7) #53 $stop;
end
endmodule
```



## Part 5

```


`timescale 1ns/1ns
module myNOT(input a, output b);
supply1 vdd;
supply0 gnd;
pmos #(5, 6, 7) T1(b, vdd, a);
nmos #(3, 4, 5) T2(b, gnd, a);
endmodule

module function_g(input[1:0] A, input[1:0] B, output g);
wire i, j, a0, a1, b0, b1;
myNOT N1(.a(A[0]), .b(a0));
myNOT N2(.a(B[0]), .b(b0));
myNOT N3(.a(B[1]), .b(b1));
myOAI_boolalg OAI1(.a(A[1]), .b(b1), .c(b0), .w(i));
myOAI_boolalg OA2(.a(A[1]), .b(A[1]), .c(b1), .w(j));
myOAI_boolalg OA3(.a(a0), .b(i), .c(j), .w(g));
endmodule

```
 
## Part 6

```
`timescale 1ns/1ns
module TB_6();
logic [1:0] A, B;
wire g;
function_g cutG(A, B, g);
initial begin
for (int i = 0; i < 4; i++) begin
for (int j = 0; j < 4; j++) begin
A = i[1:0];
B = j[1:0];
#271;
end
end
endmodule;
```



## Essential

ModelSim - INTEL FPGA STARTER EDITION 2020.1

File Edit View Compile Simulate Add Source Tools Layout Bookmarks Window Help

ColumnLayout AllColumns

Project - D:\ModelSim\CA1\CA1

Name	Status	Type	Order	Modified
TB_3.sv	✓	Syst...	8	03/12/2025 07:36:34
nor_sw.sv	✓	Syst...	0	03/12/2025 08:03:18
oa_ba.sv	✓	Syst...	2	03/12/2025 07:34:45
nor_tb.sv	✓	Syst...	1	03/11/2025 11:11:11
TB_2.sv	✓	Syst...	7	03/12/2025 12:12:49
oa_norgate.sv	✓	Syst...	3	03/12/2025 12:06:05
TB_4.sv	✓	Syst...	9	03/12/2025 07:55:06
oa_sw.sv	✓	Syst...	4	03/11/2025 11:37:13
TB_6.sv	✓	Syst...	11	03/12/2025 10:19:31
function_g.sv	✓	Syst...	10	03/12/2025 10:40:28
TB_1.sv	✓	Syst...	6	03/12/2025 08:54:20
oa_tb.sv	✓	Syst...	5	03/11/2025 11:57:21

D:\ModelSim\CA1\TB\_6.sv (TB\_6) - Default

```
1 timescale 1ns/1ns
2 module TB_6();
3 logic [1:0] A, B;
4 wire g;
5 function_g_outG(A, B, g);
6 initial begin
7   for (int i = 0; i < 4; i++) begin
8     for (int j = 0; j < 4; j++) begin
9       A = i[1:0];
10      B = j[1:0];
11      #27;
12    end
13  end
14 end
15 endmodule;
16
17
```

Library Project

Transcript

```
# Compile of TB_2.sv was successful.
# Compile of TB_3.sv was successful.
# Compile of TB_4.sv was successful.
# Compile of function_g.sv failed with 1 errors.
# Compile of TB_6.sv was successful with warnings.
# 12 compiles, 1 failed with 1 error.
# Compile of nor_sw.sv was successful.
```

Ln: 16 Col: 0 Project: CA1 <No Design Loaded> <No Context>